


DC POWER SUPPLY

BUCK CONVERTER


# DC POWER SUPPLY

## Buck converter – basic concepts

- The circuit:

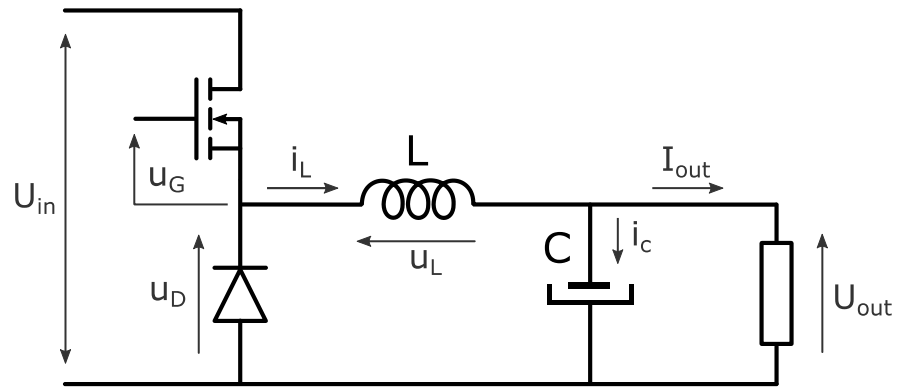

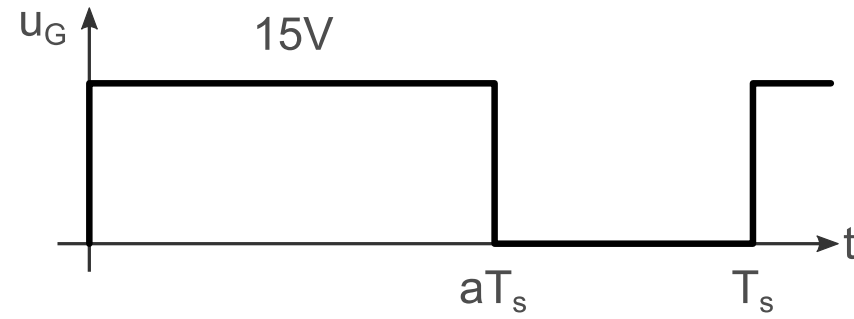- Modulation: Pulse width modulation (PWM)




$T_s$  – switching period

$f_s = 1/T_s$  – switching frequency

$a$  – duty cycle

# DC POWER SUPPLY

## Assumptions and approximations

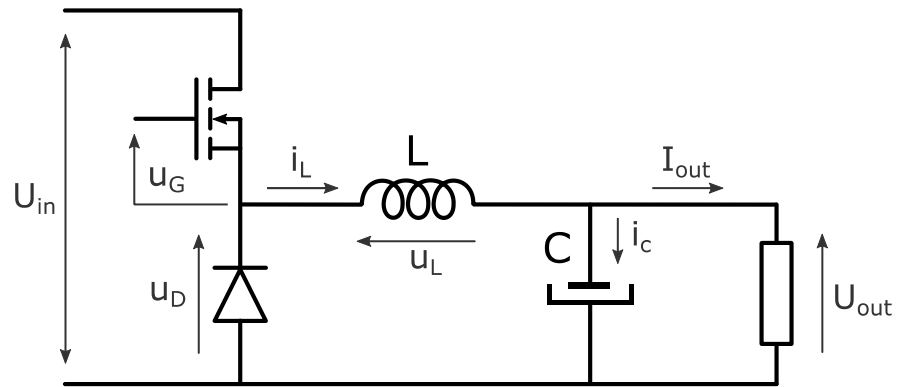


- Assumptions of importance DC power supply analysis:
  - Input voltage ( $U_{in}$ ) oscillations can be neglected, within  $T_s$  period.
  - Output voltage ( $U_{out}$ ) oscillations can be neglected while addressing other variables in the circuit ( $\Delta U_{out} \ll U_{out}$ ).
  - Output current ( $I_{out}$ ) oscillations can be neglected while addressing other variables in the circuit.
  - Parasitic elements (L,C) are neglected.
  - Resistances of the L and C are neglected.
  - Skin effect is not considered...

# DC POWER SUPPLY



## Assumptions and approximations

- Steady state:

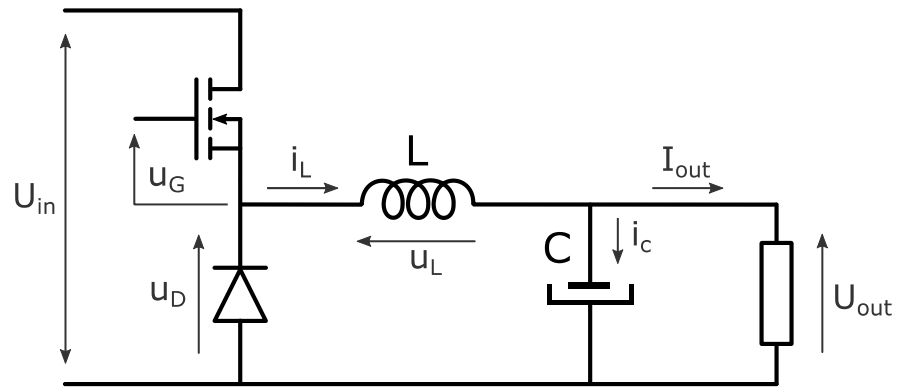



# DC POWER SUPPLY

## Buck - operation

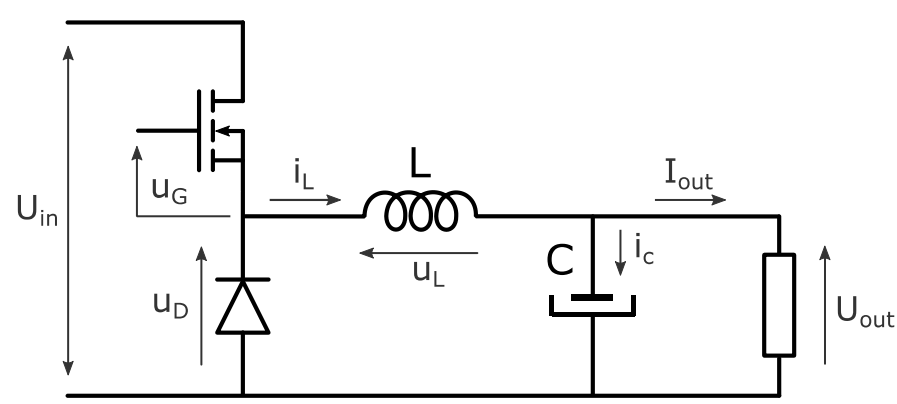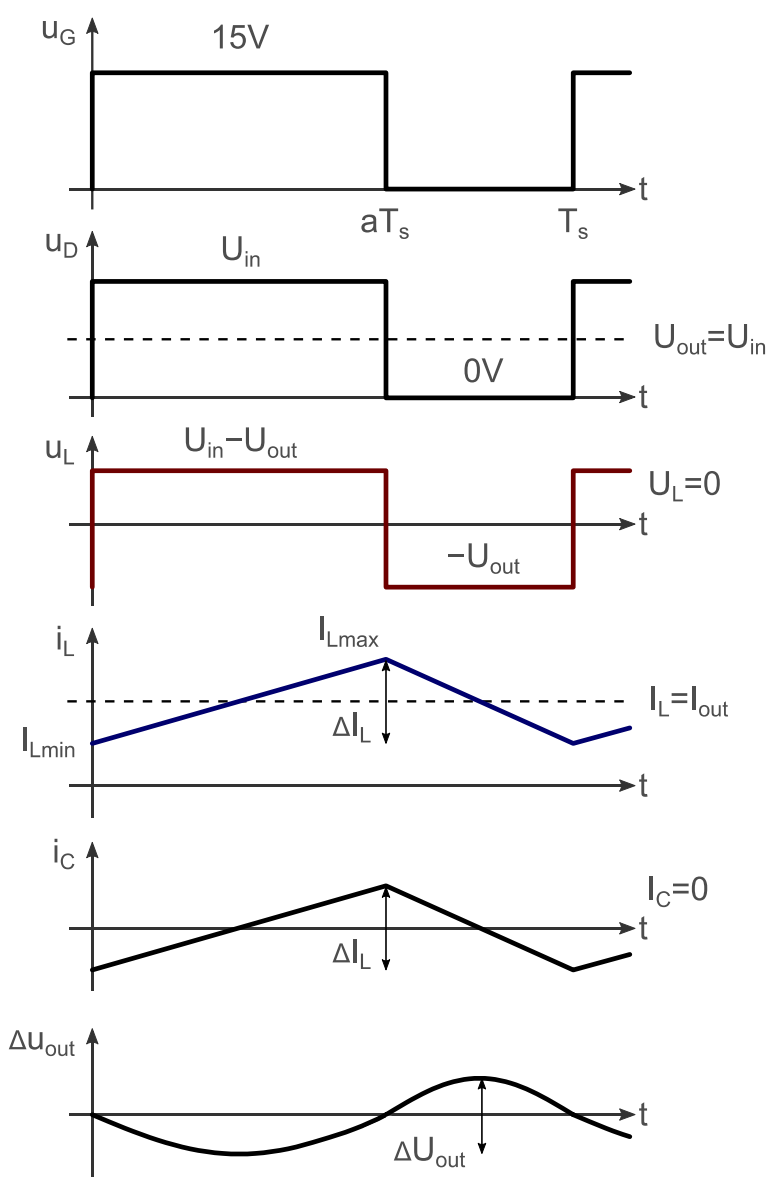


# DC POWER SUPPLY

## Buck - continuous conduction mode

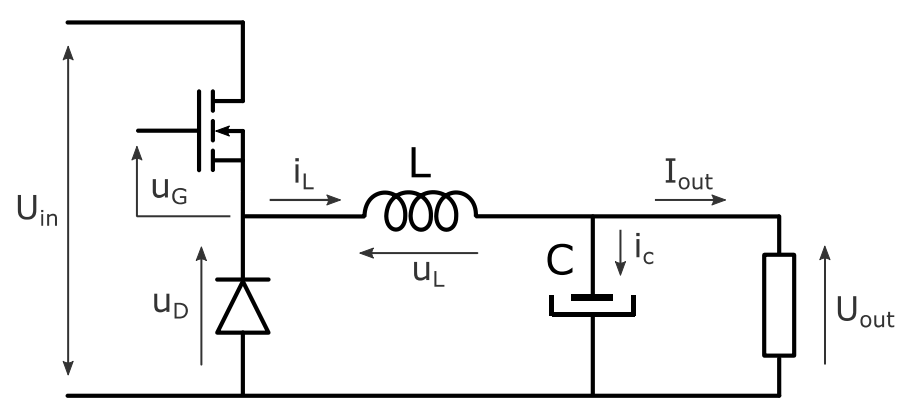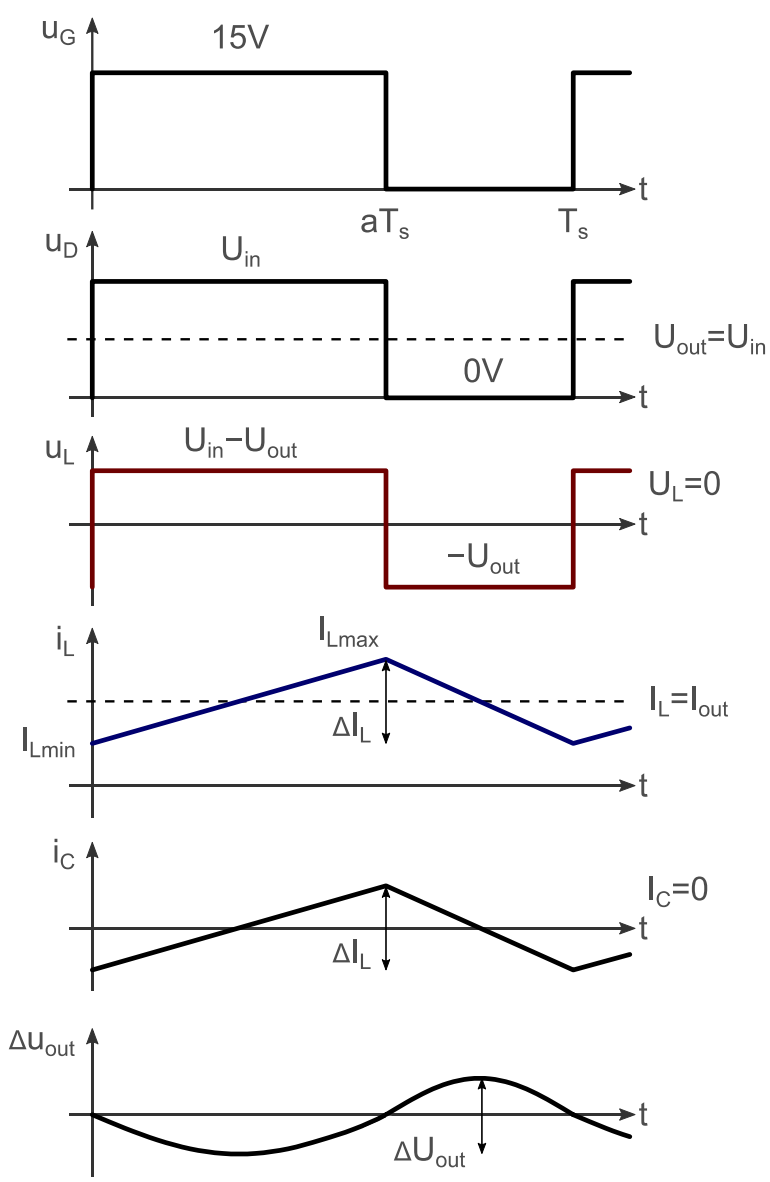

# DC POWER SUPPLY

## Buck - continuous conduction mode

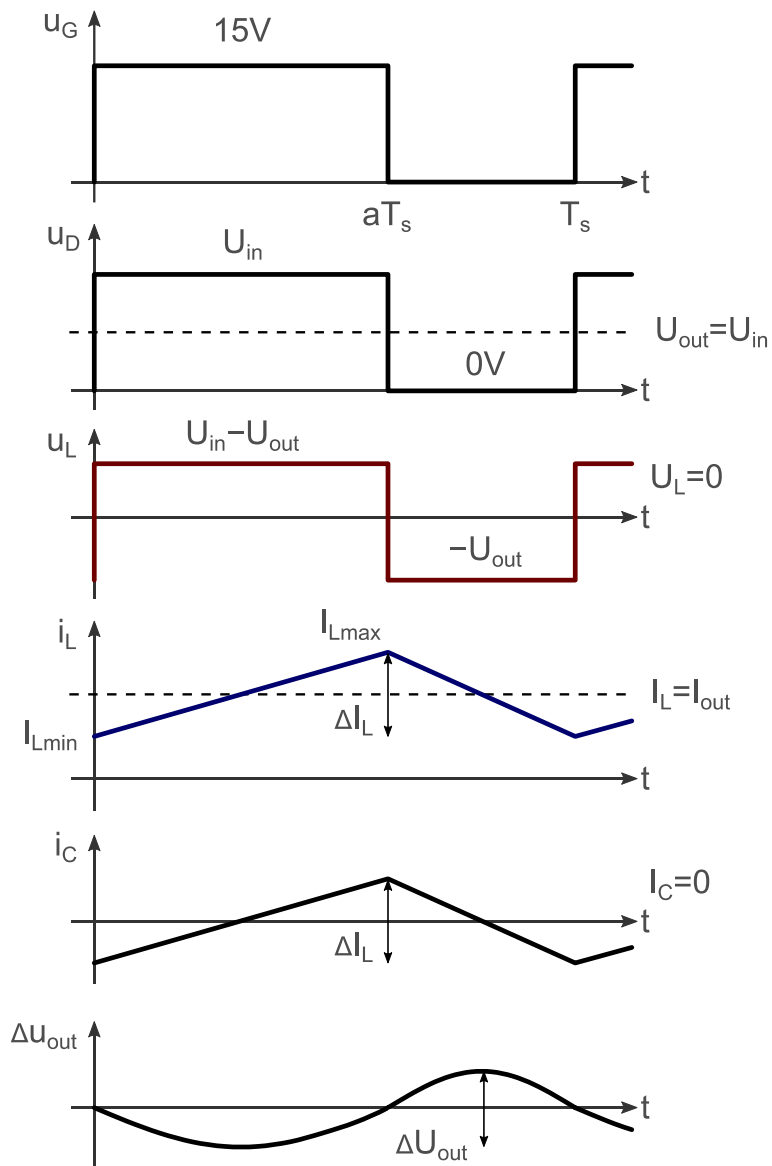


- *Current "turns-ratio"*

$$P_{in} = P_{out}$$

$$\Rightarrow U_{in} \cdot I_{in} = U_{out} \cdot I_{out}$$

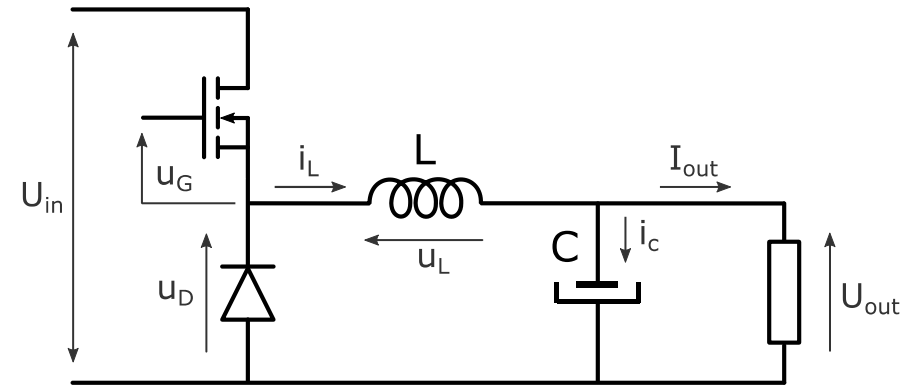
$$\Rightarrow \frac{I_{out}}{I_{in}} = \frac{U_{in}}{U_{out}} = \frac{1}{a}$$



# DC POWER SUPPLY

## Buck - continuous conduction mode

### Output filter (LC) design

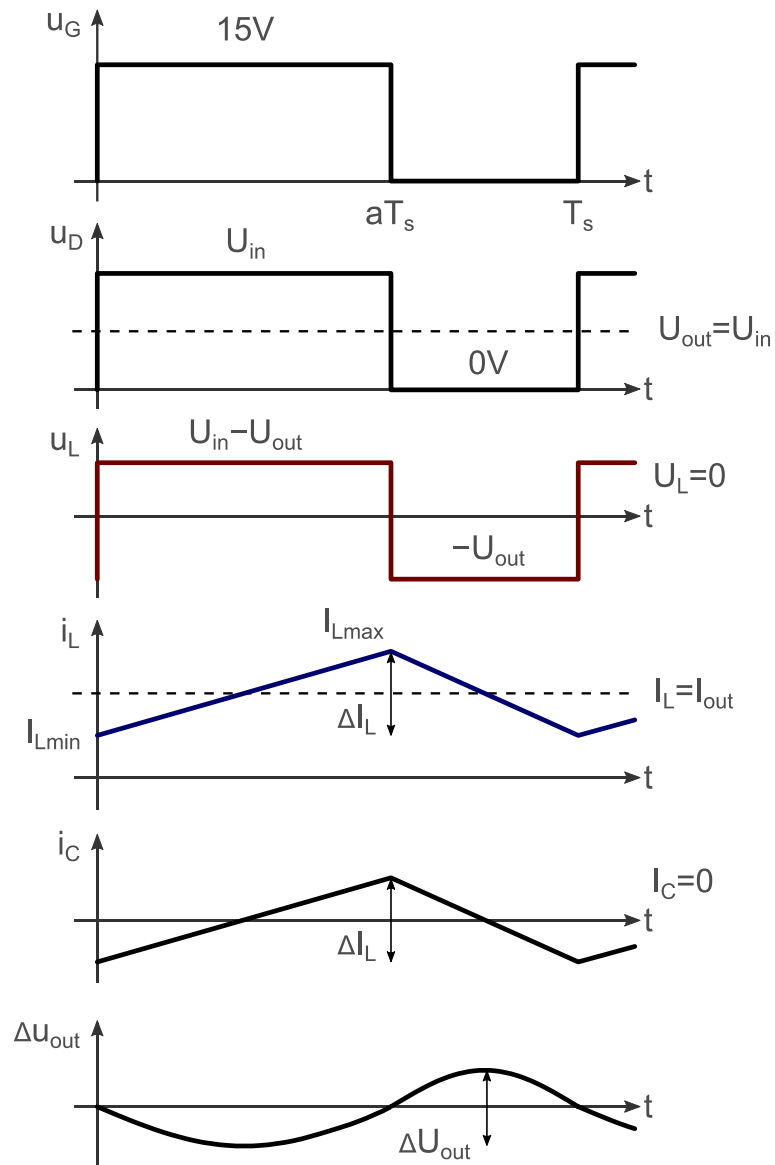

- Inductance:

Continuous conduction mode condition:


$$I_L \geq \frac{\Delta I_L}{2}$$



# DC POWER SUPPLY

## Buck - continuous conduction mode

### Output filter (LC) design

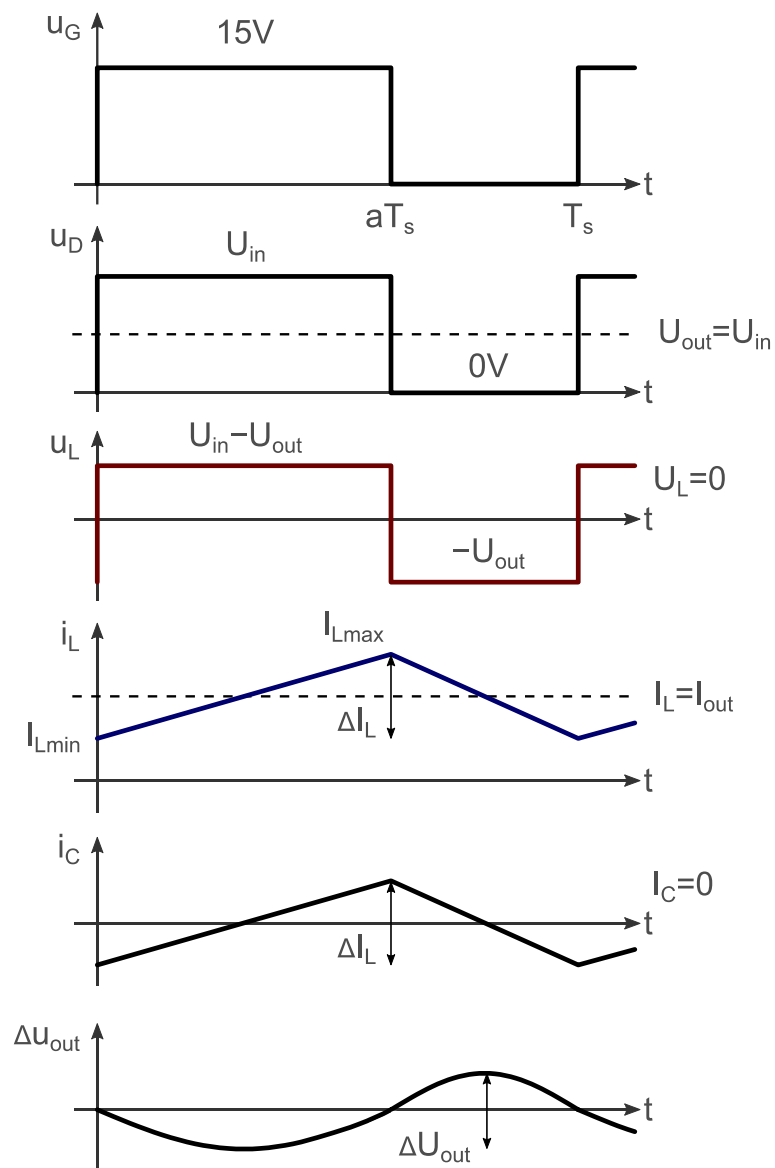

- Inductance:

**Continuous conduction mode condition:**

$$I_{out} \geq \frac{1}{2} \cdot \frac{U_{out} \cdot (1 - a)T_s}{L} \Rightarrow$$
$$L \geq \frac{U_{out} \cdot (1 - a)T_s}{2 \cdot I_{out}}$$

Inductor choice:


$$a = a_{min}, \quad I_{out} = I_{outmin}$$

$$\Rightarrow L \geq \frac{U_{out} \cdot T_s}{2 \cdot I_{outmin}} \cdot \left(1 - \frac{U_{out}}{U_{inmax}}\right)$$

# DC POWER SUPPLY

## Buck - continuous conduction mode



### Output filter (LC) design

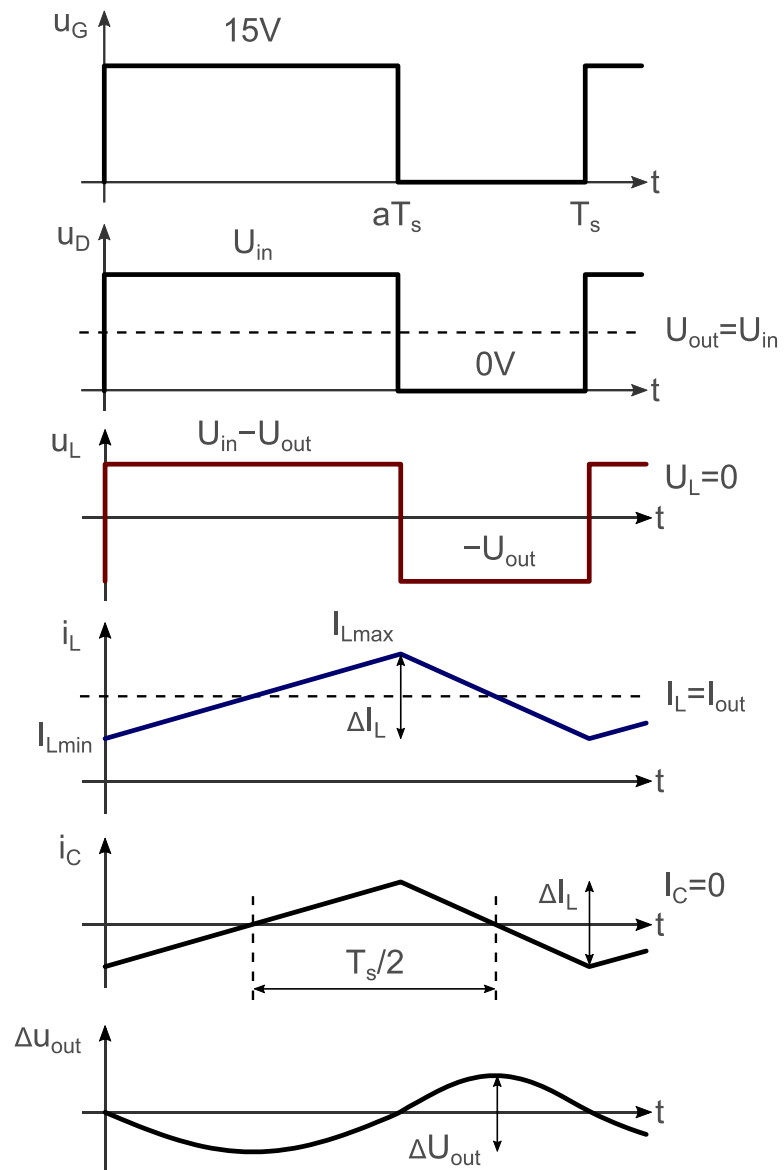

- Capacitance:

# DC POWER SUPPLY

## Buck - discontinuous conduction mode

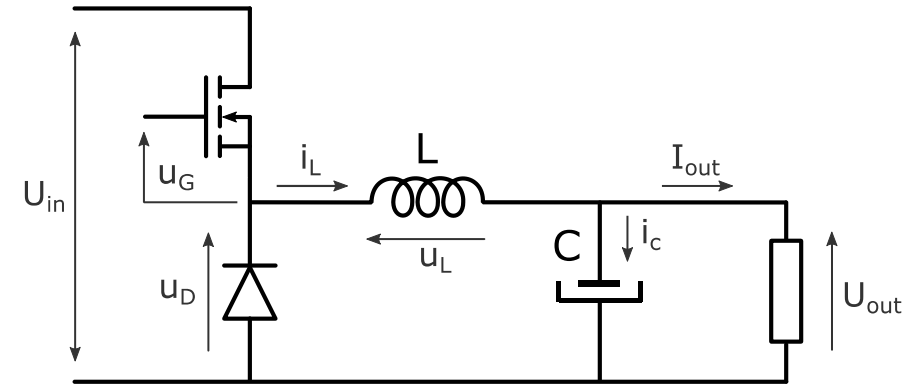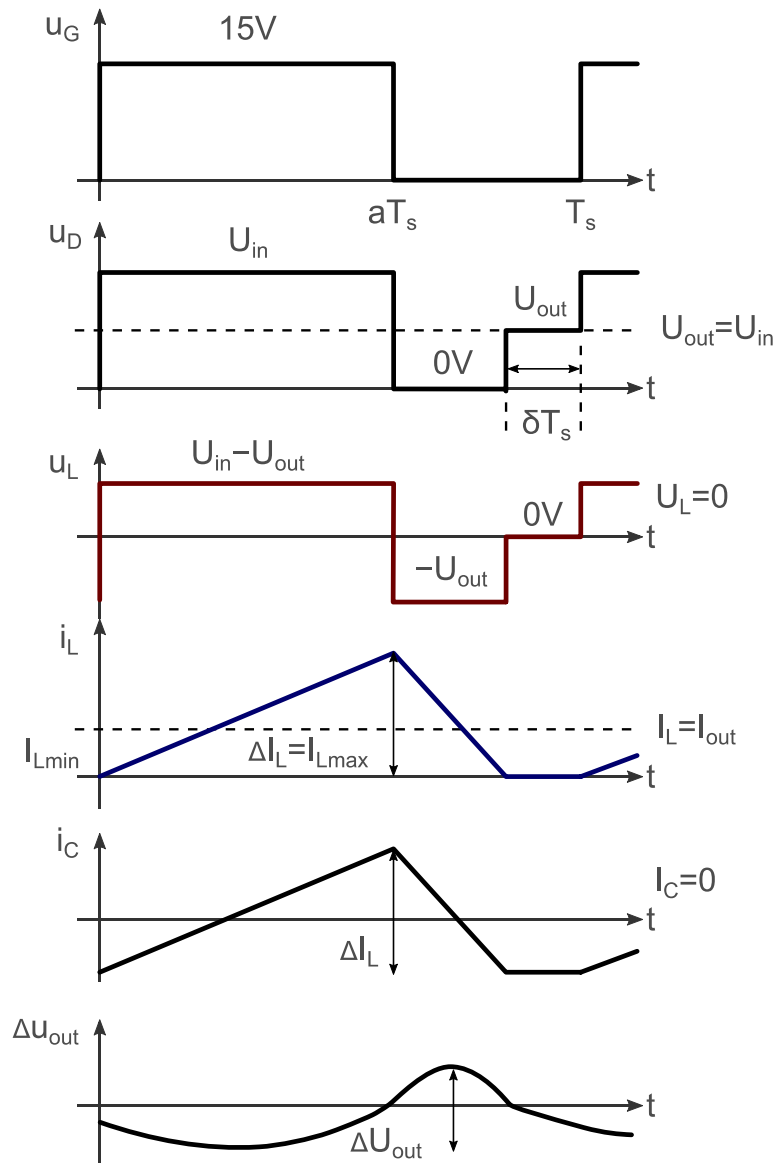

- *Voltage "turns-ratio"*


$$U_L = 0 \Rightarrow (U_{in} - U_{out}) \cdot aT_s = U_{out} \cdot (1 - a - \delta)T_s$$

$$\Rightarrow \frac{U_{out}}{U_{in}} = \frac{a}{1 - \delta}$$

$$\Rightarrow \frac{I_{out}}{I_{in}} = \frac{U_{in}}{U_{out}} = \frac{1 - \delta}{a}$$

# DC POWER SUPPLY


## Buck - discontinuous conduction mode

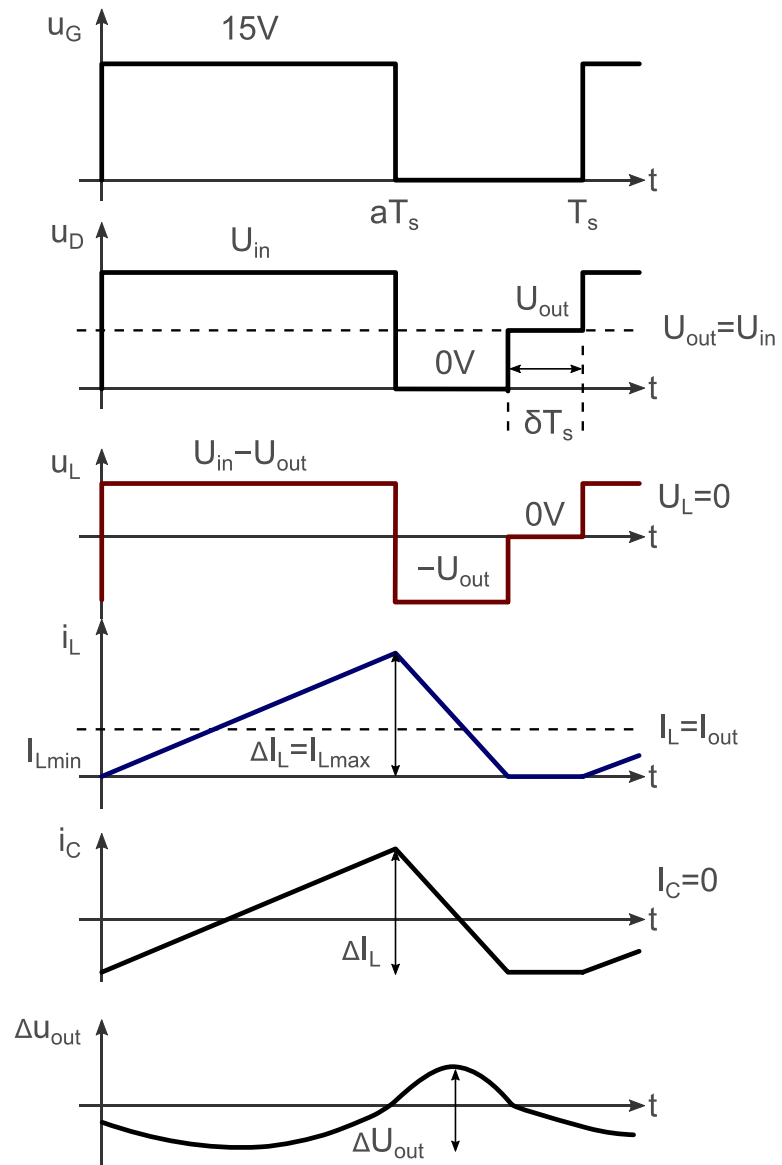

- Duty cycle expression using known variables

# DC POWER SUPPLY

## Buck - discontinuous conduction mode

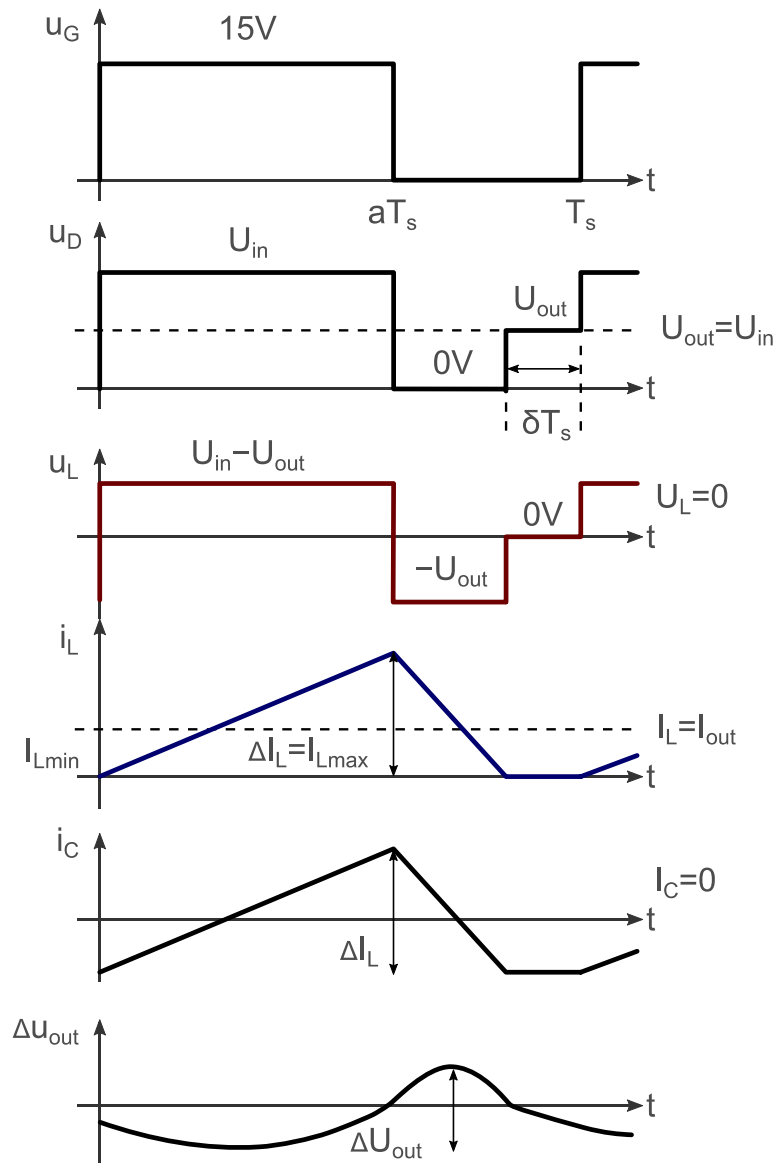

- Duty cycle expression using known variables

$$\frac{U_{out}}{U_{in}} = \frac{a}{1 - \delta} \quad (1)$$

$$I_{Lmax} = \frac{U_{out} \cdot (1 - a - \delta) T_s}{L} \quad (2)$$


$$I_L = I_{out} = I_{Lmax} \cdot \frac{1 - \delta}{2} \quad (3)$$

$$\Rightarrow a^2 = \frac{2 \cdot L \cdot I_{out}}{T_s} \left( \frac{U_{out}}{U_{in}} \cdot \frac{1}{U_{in} - U_{out}} \right)$$

# DC POWER SUPPLY


## Buck - boundary operation

- Boundary condition:

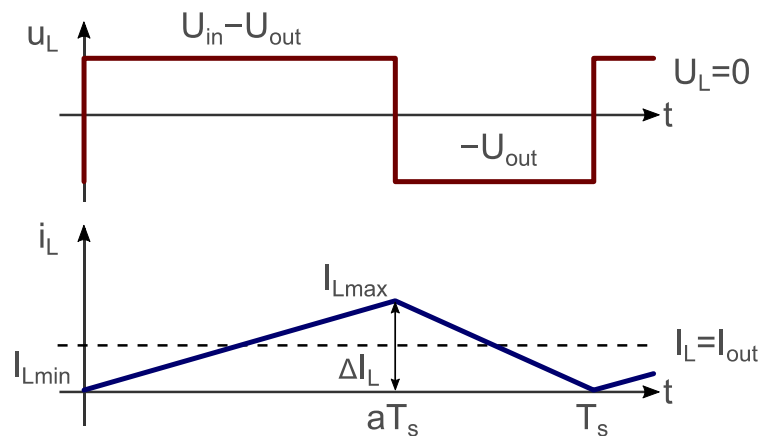

$$I_{outb} = \frac{I_{Lmax}}{2} = \frac{U_{out} \cdot (1 - a)T_s}{2L}$$

- Operating area:

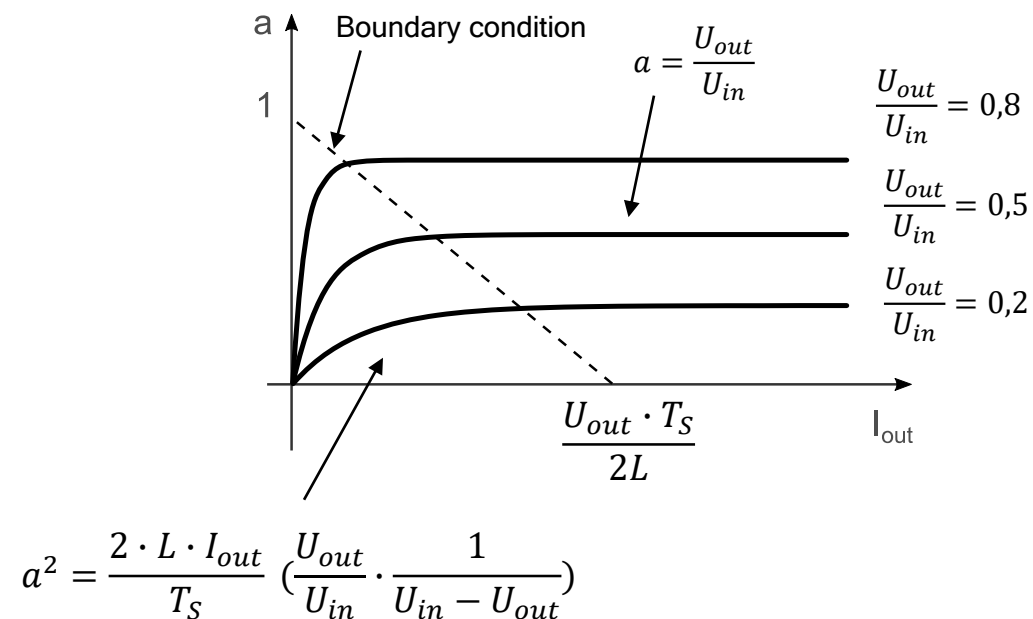

$$a^2 = \frac{2 \cdot L \cdot I_{out}}{T_s} \left( \frac{U_{out}}{U_{in}} \cdot \frac{1}{U_{in} - U_{out}} \right)$$