


Elementary circuits 2


- How circuits with controllable devices behave?
- What is a freewheeling diode?


Elementary transistor circuits

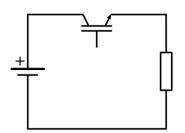


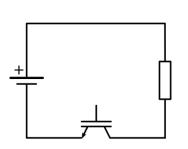

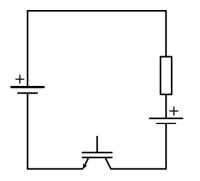


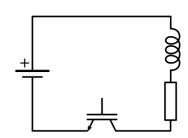


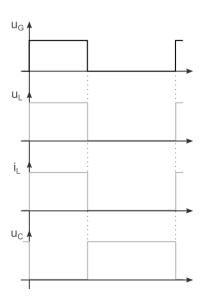


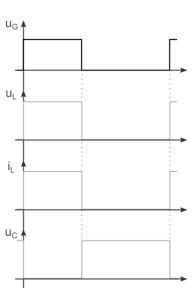

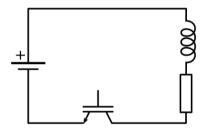Elementary transistor circuits - freewheeling diode



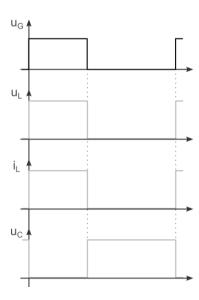

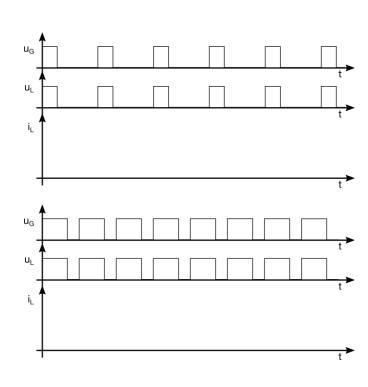

Elementary transistor circuits - freewheeling diode

